

Part A

1 a. $20 + 30 + 50 = \underline{100 \Omega}$

b. $\frac{1}{R_T} = \frac{1}{20} + \frac{1}{100} + \frac{1}{50} = \frac{5+1+2}{100} = \frac{8}{100} = \frac{1}{R_T} \quad \frac{8R_T}{8} = \frac{100 \Omega}{8} = 12.5$
 $= \underline{12.5 \Omega}$

2. Current = $\frac{\text{Voltage}}{\text{Resistance}}$

a. $\frac{125}{100} = \underline{1.25 A}$

b. $\frac{12.5}{125} = \frac{125 \times 10}{125} = \underline{10 A}$

3. a. $I_T \cdot I_1 = I_2 + I_3 = \underline{1.25 A}$

b. $\frac{125}{20} + \frac{125}{100} + \frac{125}{50} = 6.25 A + 1.25 + 2.5 = \underline{10 A}$

4 a. Voltage = $I \times R$

$1.25 \times 20 = 25$

$1.25 \times 30 = 37.5$

$1.25 \times 50 = 62.5$

$$\begin{array}{r} 25 \\ + 37.5 \\ + 62.5 \\ \hline 125.0 \end{array} = \underline{125 V}$$

b. In parallel voltage is constant

$= \underline{125 V}$

5 Power dissipated

a. $P = V \times I$

$$P_{20\Omega} = 25V \times 1.25A = 31.25W$$

$$P_{30\Omega} = 37.5V \times 1.25A = 46.875W$$

$$P_{50\Omega} = 62.5V \times 1.25A = 78.125W$$

b. $P_{20\Omega} = 125V \times 6.25A = 781.25W$

$$P_{30\Omega} = 125V \times 1.25A = 156.25W$$

$$P_{50\Omega} = 125V \times 2.5A = 312.5W$$